

**Inference of
Numerical Relations from
Digital Circuits**

Enric Rodríguez-Carbonell

Jordi Cortadella

**Universitat Politècnica de Catalunya
Barcelona**

Overview of the Talk

1. **Introduction**
2. Overview of the Method
3. Simple Example: Binary Addition
4. Abstract Domain
5. Inductive Method
6. Working with Small Coefficients
7. Future Work

Introduction

Need for Hardware Verification


Errors in hardware are:

- *very costly*:
 - Pentium division bug cost Intel **0.5 billion \$**
 - Wide Field Infrared Explorer (WIRE) spacecraft from NASA failed soon after launch
- *irreversible*: no patches possible once product is on market

Need for Hardware Verification to Increase Reliability !

Introduction

Verifying Hardware

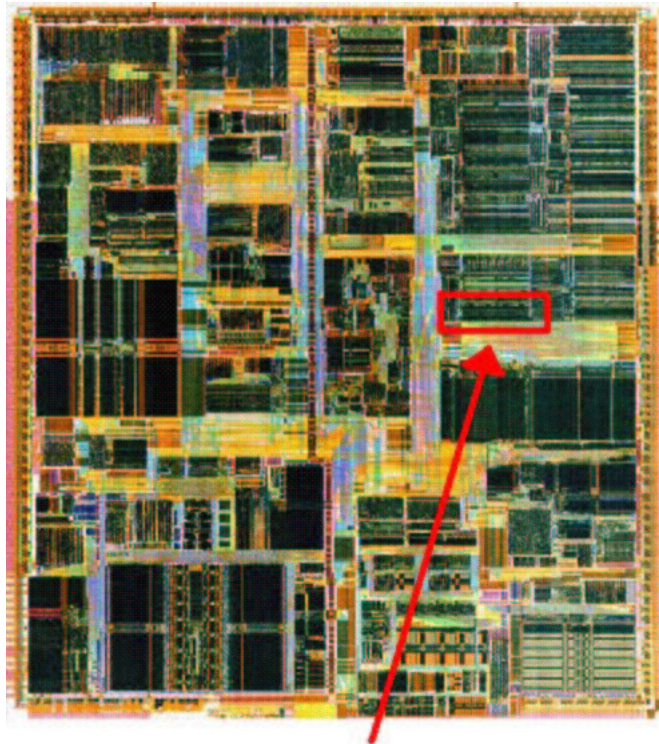


64-bit adder

- When verifying hardware we have:
 - Gate list
 - High-level specification
- **PROBLEM:** Huge gap !
- **SOLUTION:** Abstraction
Reverse engineering discovers properties hidden in circuits

Introduction

Abstracting Circuits

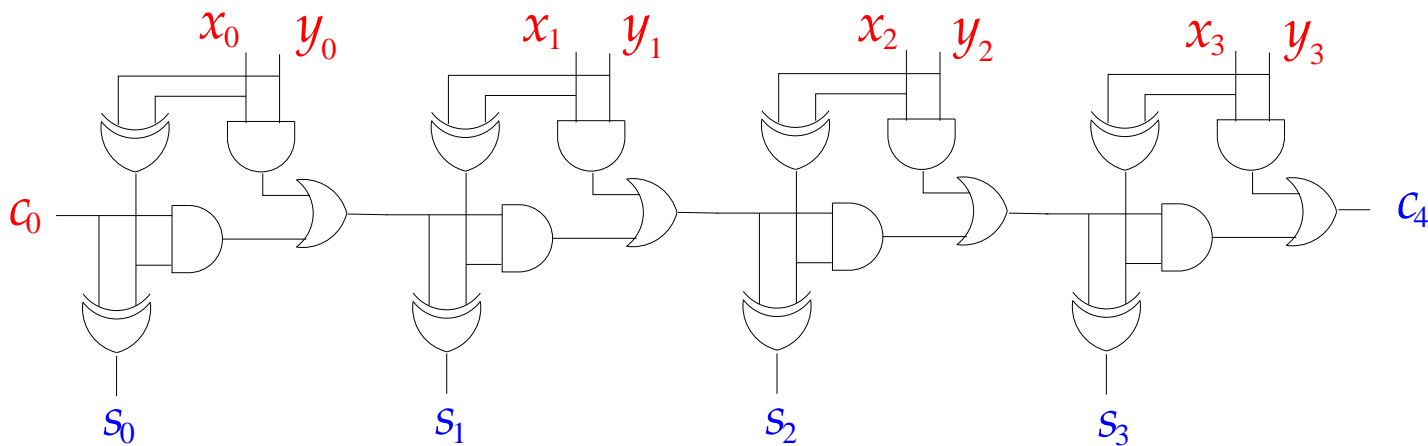

\bar{x} , \bar{y} , \bar{s} : 4-bit integers

$$\bar{s} + 16c_4 = c_0 + \bar{x} + \bar{y}$$

Introduction

Arithmetic Circuits are Difficult

- Arithmetic circuits are **difficult to verify**
- **BDD's** representing multipliers have **huge size**
- Current techniques **cannot handle** real-sized **multipliers**
- **Arithmetics** has **not been sufficiently exploited**

⇒ Combination logics/arithmetics

Overview of the Talk

1. Introduction
2. **Overview of the Method**
3. Simple Example: Binary Addition
4. Abstract Domain
5. Inductive Method
6. Working with Small Coefficients
7. Future Work

Overview of the Method


- **GOAL:** extract numerical relations from arithmetic circuits
- **APPLICATION:** preprocessing step to alleviate formal verification with other methods
- **Boolean values** abstracted to **integers**
- **Boolean functions** abstracted to **polynomials**
- **Gaussian elimination** used to infer numerical relations

Overview of the Talk

1. Introduction
2. Overview of the Method
3. **Simple Example: Binary Addition**
4. Abstract Domain
5. Inductive Method
6. Working with Small Coefficients
7. Future Work

Simple Example: Binary Addition

Full Adder

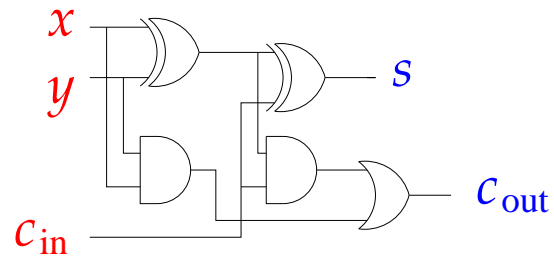

- Full adder: sum of two bits with carry in and carry out
- Input signals: x , y , c_{in}
- Output signals: s , c_{out}
- **GOAL**: generate the equation

$$s + 2c_{out} = x + y + c_{in}$$

Simple Example: Binary Addition

From Boolean Functions to Polynomials

$$\begin{aligned}
 x \text{ AND } y &= xy \\
 x \text{ XOR } y &= x + y - 2xy \\
 x \text{ OR } y &= x + y - xy \\
 \text{NOT } x &= 1 - x
 \end{aligned}$$

$$x \in \{0, 1\} \implies x^2 = x$$

$$\begin{aligned}
 s &= x \text{ XOR } y \text{ XOR } c_{in} \\
 c_{out} &= (x \text{ AND } y) \text{ OR } (x \text{ AND } c_{in}) \text{ OR } (y \text{ AND } c_{in})
 \end{aligned}$$

$$\begin{aligned}
 s &= x + y - 2xy + c_{in} - 2c_{in}x - 2c_{in}y + 4c_{in}xy \\
 c_{out} &= xy + c_{in}x + c_{in}y - c_{in}^2xy - x^2yc_{in} - xy^2c_{in} + x^2y^2c_{in}^2
 \end{aligned}$$

$$\begin{aligned}
 s &= x + y - 2xy + c_{in} - 2c_{in}x - 2c_{in}y + 4c_{in}xy \\
 c_{out} &= xy + c_{in}x + c_{in}y - 2c_{in}xy
 \end{aligned}$$

Simple Example: Binary Addition

Applying Gaussian Elimination

- Non-linear terms are considered as new variables
- Variables eliminated using Gaussian elimination

$$\begin{aligned} s &= x + y + c_{in} - 2xy - 2c_{in}x - 2c_{in}y + 4c_{in}xy \\ c_{out} &= xy + c_{in}x + c_{in}y - 2c_{in}xy \end{aligned}$$

↓

$$s + 2c_{out} = x + y + c_{in}$$

- Sometimes the aimed equation has non-linear terms:
for carry look-ahead,

$$2^n \cdot (G + Pc_{in}) + \sum_{i=0}^{n-1} 2^i s_i = c_{in} + \sum_{i=0}^{n-1} 2^i (x_i + y_i)$$

→ Heuristics to select the terms to be eliminated

Overview of the Talk

1. Introduction
2. Overview of the Method
3. Simple Example: Binary Addition
4. **Abstract Domain**
5. Inductive Method
6. Working with Small Coefficients
7. Future Work

Abstract Domain

- ABSTRACT VALUES:

vector spaces of polynomials with coefficients in \mathbb{Q}

- ABSTRACTION FUNCTION α

$$\begin{aligned} \alpha : \mathcal{P}(\{0, 1\}^n) &\longrightarrow \{\text{vector spaces in } \mathbb{Q}[x_1, \dots, x_n]\} \\ B &\longmapsto \{\text{vector space of} \\ &\quad \text{polynomials evaluating to 0 on } B\} \end{aligned}$$

- CONCRETIZATION FUNCTION γ

$$\begin{aligned} \gamma : \{\text{vector spaces in } \mathbb{Q}[x_1, \dots, x_n]\} &\longrightarrow \mathcal{P}(\{0, 1\}^n) \\ V &\longmapsto \{\text{zeros of } V \text{ in } \{0, 1\}^n\} \end{aligned}$$

Abstract Domain

Equations of output variables as \longrightarrow Polynomial
boolean functions of input variables \longrightarrow equations

- Not all consequences of equations are linear combinations
 - **Linear algebra not complete !!**
 - **Ideals of polynomials (Gröbner bases) bad complexity**
- **INTERMEDIATE SOLUTION:**
 - approximate ideal generated by equations
 - add new equations by multiplying by monomials, using $x_i^2 = x_i$

\longrightarrow Heuristics to select new equations to add


Overview of the Talk

1. Introduction
2. Overview of the Method
3. Simple Example: Binary Addition
4. Abstract Domain
5. **Inductive Method**
6. Working with Small Coefficients
7. Future Work

Inductive Method

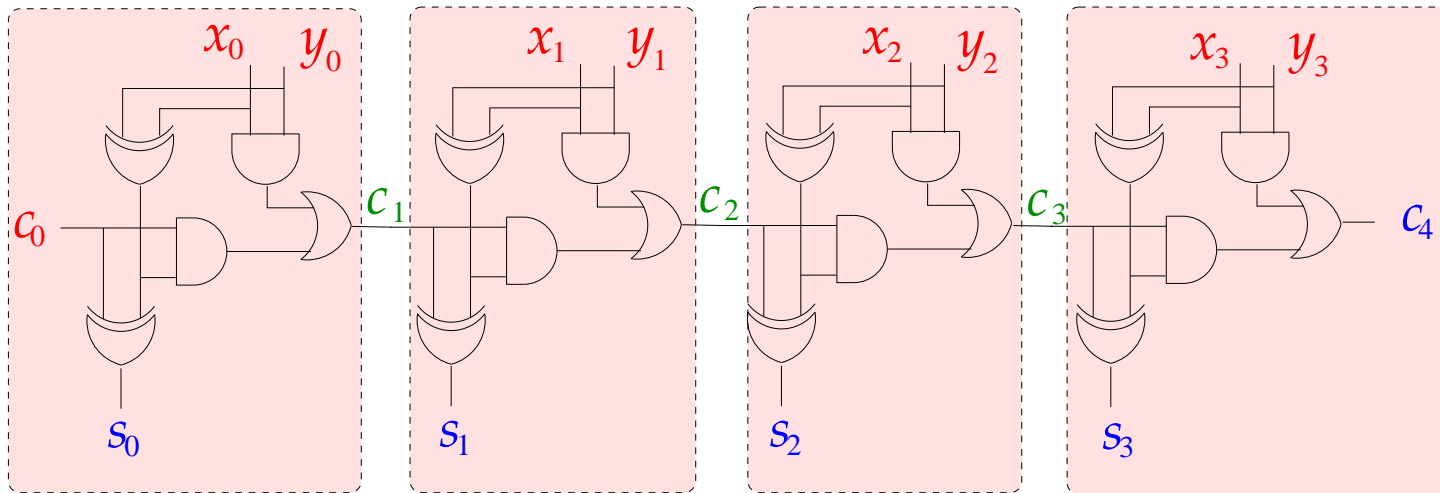- **PROBLEM:** Not feasible for big number of variables
- **SOLUTION:**
 - Decompose circuit into black-boxes inductively
 - Behaviour of black boxes described by polynomials
 - Bigger black boxes built from smaller black boxes
 - *Local signals* (neither *input* nor *output*) eliminated by Gaussian elimination

Inductive Method Example: 4-bit Carry-Ripple Adder



$$s_0 + 2c_1 = c_0 + x_0 + y_0$$

$$s_1 + 2c_2 = c_1 + x_1 + y_1$$

$$s_2 + 2c_3 = c_2 + x_2 + y_2$$

$$s_3 + 2c_4 = c_3 + x_3 + y_3$$

$$s_0 + 2s_1 + 4s_2 + 8s_3 + 16c_4 = c_0 + x_0 + 2x_1 + 4x_2 + 8x_3 + y_0 + 2y_1 + 4y_2 + 8y_3$$

$$\bar{s} + 16c_4 = c_0 + \bar{x} + \bar{y}$$

Overview of the Talk

1. **Introduction**
2. **Overview of the Method**
3. **Simple Example: Binary Addition**
4. **Abstract Domain**
5. **Inductive Method**
6. **Working with Small Coefficients**
7. **Future Work**

Working with Small Coefficients

- **Coefficients** in numerical relations we are interested are $\pm 2^i$
- **Coefficients** may be **very large** in computations
 - Exact arithmetic is **slow**
 - Risk of **overflow**
- **Use finite fields for the coefficients !**
- **Advantages:**
 - **Coefficients** can be represented with **few bits**
 - **Arithmetics** can be **tabulated** at compile-time
- **Disadvantages:**
 - **Not sound**
 - ... but results can be later checked

Working with Small Coefficients

- Let p be an odd prime number such that 2 generates \mathbb{Z}_p^*
- There are **many** such prime numbers
- Let $q = (p - 3)/2$. Then:

$$\mathbb{Z}_p^* = \{-2^q, -2^{q-1}, \dots, -2^2, -2, -1, 1, 1, 2, 2^2, \dots, 2^q\}$$

- Heuristic approach:
 1. Work with polynomials with **coefficients in the finite field**
 2. Once result computed, **translate back** into coefficients as powers of 2

Working with Small Coefficients

$\pm 2^i$	Z_{19}^*
-256	10
-128	5
-64	12
-32	6
-16	3
-8	11
-4	15
-2	17
-1	18
1	1
2	2
4	4
8	8
16	16
32	13
64	7
128	14
256	9

8-BIT ADDER

$$s_0 + 2s_1 + 4s_2 + 8s_3 + 16s_4 + 13s_5 + 7s_6 + 14s_7 + 10c_4 = c_0 + x_0 + 2x_1 + 4x_2 + 8x_3 + 16x_4 + 13x_5 + 7x_6 + 14x_7 + y_0 + 2y_1 + 4y_2 + 8y_3 + 16y_4 + 13y_5 + 7y_6 + 14y_7$$



$$s_0 + 2s_1 + 4s_2 + 8s_3 + 16s_4 + 32s_5 + 64s_6 + 128s_7 + 256c_4 = c_0 + x_0 + 2x_1 + 4x_2 + 8x_3 + 16x_4 + 32x_5 + 64x_6 + 128x_7 + y_0 + 2y_1 + 4y_2 + 8y_3 + 16y_4 + 32y_5 + 64y_6 + 128y_7$$

Overview of the Talk

1. **Introduction**
2. **Overview of the Method**
3. **Simple Example: Binary Addition**
4. **Abstract Domain**
5. **Inductive Method**
6. **Working with Small Coefficients**
7. **Future Work**

Future Work

- Heuristics for eliminating terms in Gaussian elimination
- Heuristics for adding new equations
- Implementation in progress
- Regularity-based techniques for partitioning circuits
- Application to adders and multipliers
- Integration to a verification system